

Exam

Name _____

- 1) $X = ABC + BCD$ is in the form of a sum-of-products expression. 1) _____
- 2) NAND gates cannot be used to construct NOR gates. 2) _____
- 3) $\overline{AB} = \overline{A} + \overline{B}$? 3) _____
- 4) The expression $A \oplus B$ represents _____. 4) _____
 - A) the sum output of a half-adder
 - B) the carry output of a half-adder
 - C) the carry output of a full-adder
 - D) the sum output of a full-adder

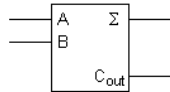


Figure 6-1

- 5) Referring to the symbol in Figure 6-1, which combination of outputs should never occur? 5) _____
 - A) $\Sigma = 1, C_{out} = 1$
 - B) $\Sigma = 0, C_{out} = 1$
 - C) $\Sigma = 1, C_{out} = 0$
 - D) $\Sigma = 0, C_{out} = 0$
- 6) The expression $(A \oplus B) \oplus C_{in}$ describes _____. 6) _____
 - A) the sum output of a full-adder
 - B) the carry output of a full-adder
 - C) the sum output of a half-adder
 - D) the carry output of a half-adder
- 7) The expression $AB + (A \oplus B)C_{in}$ describes _____. 7) _____
 - A) the carry output of a full-adder
 - B) the sum output of a full-adder
 - C) the sum output of a half-adder
 - D) the carry output of a half-adder


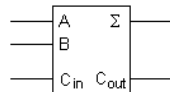


Figure 6-2


- 8) The symbol in Figure 6-2 represents a(n) _____. 8) _____
 - A) And function
 - B) full-adder
 - C) PLD
 - D) half-adder
- 9) Refer to the symbol in Figure 6-2. What are the output when $A = 1, B = 1, C_{in} = 1$? 9) _____
 - A) $\Sigma = 0, C_{out} = 1$
 - B) $\Sigma = 1, C_{out} = 1$
 - C) $\Sigma = 0, C_{out} = 0$
 - D) $\Sigma = 1, C_{out} = 0$
- 10) A BCD-to-decimal decoder has _____ data input lines and _____ data output lines. 10) _____
 - A) 10,10
 - B) 1,10
 - C) 7,9
 - D) 4, 10

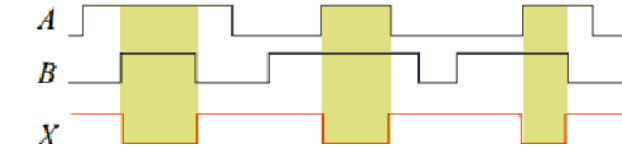- 11) A 2-input gate produces the output shown. (X represents the output.) 11) _____



- This is a(n)
 - A) NOR gate
 - B) NAND gate
 - C) OR gate
 - D) AND gate

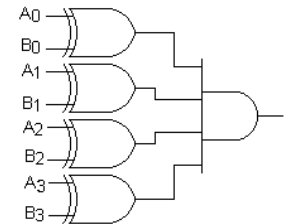
- 12) The circuit below can be used as a(n) _____. 12) _____



- A) dual 4-line multiplexer
- B) 4-bit comparator
- C) 8-bit comparator
- D) 4-bit half-adder

- 13) A multiplexer with four select, or address, lines can select one of _____ inputs. 13) _____
 - A) 15
 - B) 7
 - C) 16
 - D) 3

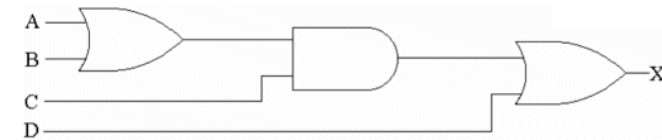- 14) For the network shown below, the boolean expression for X is _____. 14) _____



- A) $D(A + B + C)$
- B) $A + BC + D$
- C) $((A + B) \cdot C) + D$
- D) $(AC + BC)D$

15) The simplest Boolean expression for the Karnaugh map below is _____.

15) _____

		\bar{C}	C
\bar{A}	\bar{B}	0	0
\bar{A}	B	1	1
A	B	1	1
A	\bar{B}	0	1

- A) $ABC + ABC + A\bar{B}C$ B) $X = AC + B$
 C) $X = A\bar{B}$ D) $AB + A\bar{B}$

16) Which of the truth tables below describes the Exclusive-NOR gate?


16) _____

A	B	X	A	B	X	A	B	X	A	B	X
0	0	1	0	0	1	0	0	0	0	0	1
0	1	0	0	1	1	0	1	1	0	1	0
1	0	0	1	0	1	1	0	1	1	0	0
1	1	1	1	1	0	1	1	0	1	1	0

- (A) (B) (C) (D)
 A) (A) B) (B) C) (C) D) (D)

17) The timing diagram below is correct for a 2-input _____ gate.

17) _____

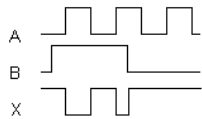

- A) AND B) OR C) NAND D) Exclusive-OR


18) A device that is used to switch one of several input lines to a single output line is called a _____
 A) decoder B) comparator C) multiplexer D) demultiplexer

19) Which of the following is an invalid BCD code?
 A) 0101 B) 1001 C) 0011 D) 1101

20) A BCD-to-decimal decoder has _____ data input lines and _____ data output lines.
 A) 1,10 B) 10,10 C) 4, 10 D) 7,9

21) If the data select lines of the MUX are $S_1S_0 = 01$, the output will be

21) _____

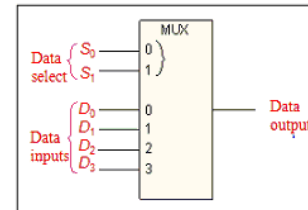

- A) equal to D_1 B) HIGH C) equal to D_0 D) LOW

22) What is the BCD form of decimal 834?
 A) 100001110100 B) 010000111000 C) 100001101000 D) 1101000010

Answer Key

Testname: TEST_C6

- 1) TRUE
- 2) FALSE
- 3) TRUE
- 4) A
- 5) A
- 6) A
- 7) A
- 8) B
- 9) B
- 10) D
- 11) B
- 12) B
- 13) C
- 14) C
- 15) B
- 16) A
- 17) C
- 18) C
- 19) D
- 20) C
- 21) A
- 22) A