

Digital Design Laboratory

Dr. Oniga István
University of Debrecen, Faculty of Informatics

This work was supported by the construction EFOP-3.4.3-16-2016-00021.
The project was supported by the European Union, co-financed by the European Social Fund.

5. Laboratory assignments

- Comparators
- Parity generators/checkers
- Adders

Lab5_1a assignment:

Comparators for 2-bits numbers

- Create a new HDL project (Lab5_1)
 - Add a new Verilog source (Lab5_1.v)
 - Edit the Lab5_1.v file according with description bellow.
 - Add and adapt the constraints file Nexysx.UCF
 - Generate the configuration file, test the circuit and fill the table.

```
module compare_2 (output reg A_lt_B, A_gt_B, A_eq_B,  
                  input [1:0] A,B);
```

```
always @ (A or B)
begin
    A_Lt_B = 0;
    A_gt_B = 0;
    A_eq_B = 0;

    if (A==B) A_eq_B = 1;
    else if (A>B) A_gt_B = 1;
    else A_Lt_B = 1;
```

endmodule

Lab5_2: Parity generator

- Create a new HDL project (Lab5_2)
- Add a new Verilog source (Lab5_2.v) and edit it according with description bellow
- Add a new Verilog text fixture file (Lab5_2_tf.v) and add the stimulus
- Simulate the circuit

```
module oddparity_for (output reg parity, input [7:0] data);
integer k;
always@(data)
begin
    parity = 1;
    for (k = 0; k <= 7; k = k+1)
    begin
        if (data[k] == 1)
            parity = ~parity;
        end
    end
endmodule
```


```
25 module oddparity_test;
26
27     // Inputs
28     reg [7:0] data;
29
30     // Outputs
31     wire parity;
32
33     // Instantiate the Unit Under Test (UUT)
34     oddparity_for uut (
35         .parity(parity),
36         .data(data)
37     );
38     integer i;
39     initial begin
40         // Initialize Inputs
41         data = 0;
42
43         // Wait 100 ns for global reset to finish
44         #100;
45
46         for (i = 0; i <= 255; i = i+1)
47             begin
48                 #50 data = i;
49
50             end
51         end
52     end
53
54 endmodule
```

Lab5_2: Parity generator simulation





Lab5_2: Parity generator implementation

 - Add and adapt the constraints file Nexysx.UCF
- Generate the configuration file and test the circuit.




Lab5_3: 1-bit full adder

  

- Create a new HDL project (Lab5_3)
- Add a new Verilog source (half_add.v)

 
```
module half_add (output sum, carry, input a, b);
    xor (sum, a, b); // exclusive OR
    and (carry, a ,b); // AND
endmodule
```



Lab5_3a: 1-bit half adder simulation

- Add a new Verilog text fixture file (half_add_test.v)
- Specify the stimulus signals
- Simulate the circuit and verify the results
 
```
// Add stimulus here
#100
    a=1;
#100
    a=0;
    b=1;
#100
    a=1;
    b=1;
```



Lab5_3b: 1-bit full adder



Structural description of 1-bit full adder

A_i	B_i	C_{i-1}	S_i	C_i
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

$$S_i = A_i \oplus B_i \oplus C_{i-1}$$


$$C_i = A_i B_i + A_i C_{i-1} + B_i C_{i-1}$$

Full adder built from two half_adders:

  

Lab5_3b: 1-bit full adder

 - Add a new Verilog file (full_add.v)
- Specify the full adder model as in the next figure



```
module full_add (output sum_out, carry_out, input a_in, b_in, carry_in );  
  
wire w1, w2, w3;  
  
    half_add M1 (.a(a_in), .sum(w1), .b(b_in), .carry(w2));  
    half_add M2 (.sum(sum_out), .b(w1), .carry(w3), .a(carry_in));  
  
    or (carry_out, w2, w3);  
endmodule
```

Cin	A	B	Sum	Cout
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		


- Add and adapt the constraints file Nexysx.UCF
- Generate the configuration file and test the circuit.

Lab5_4: 1-bit full adder

```
// A version
module add1_full (input a, b, cin, output cout, s);
xor3_m xor(.i0(a), .i1(b), .i2(cin), .o(s));
wire a0, a1, a2;
and2_m and0(.i0(a), .i1(b), .o(a0));
and2_m and1(.i0(a), .i1(cin), .o(a1));
and2_m and2(.i0(b), .i1(cin), .o(a2));
or3_m or(.i0(a0), .i1(a1), .i2(a2), .o(cout))
endmodule
```

```
// B version
module add1_full (input a, b, cin, output cout, s);
assign s = a ^ b ^ cin;
assign cout = (a & b) | (a & cin) | (b & cin);
endmodule
```
 
```
// C version
module add1_full (input a, b, cin, output cout, s);
assign {cout, s} = a + b + cin;
endmodule
```




Cin	A	B	Sum	Cout
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

- Create a new HDL project (Lab5_4)
- Add a new Verilog source (add1_full.v). Use one of the tree source from above
- Add and adapt the constraints file Nexysx.UCF
- Generate the configuration file and test the circuit.

Lab5_5a: 4-bits adder

A 4-bit adder can be built using four 1-bit full adders

Ripple carry adder

 

- Create a new HDL project (Lab5_5a)
- Add a new Verilog source file
- Use the structural description to create a 4-bit adder (next slide)

Lab5_5a: 4-bits adder

- Create a new HDL project (Lab5_5a)
- Create a new Verilog source file add4.v with the content as bellow
- Add a copy of the source created in the previous project (add1_full.v).
- Add and adapt the constraints file Nexysx.UCF
- Generate the configuration file and test the circuit.

```
// 5_5a 4-bits adder
module add4 (input [3:0] a, b, output [4:0] s);
wire [3:0] c;
add1_full add0(.a(a[0]), .b(b[0]), .cin(1'b0), .cout(c[0]), .s(s[0]));
add1_full add1(.a(a[1]), .b(b[1]), .cin(c[0]), .cout(c[1]), .s(s[1]));
add1_full add2(.a(a[2]), .b(b[2]), .cin(c[1]), .cout(c[2]), .s(s[2]));
add1_full add3(.a(a[3]), .b(b[3]), .cin(c[2]), .cout(s[4]), .s(s[3]));
endmodule
```

Lab5_5b: 4-bits adder behavioral

- Create a new HDL project (Lab5_5b)
- Create a new Verilog source file add4.v with the content as bellow
- Add a copy of the source created in the previous project (add1_full.v).

```
// 5_5b
module add4 (input [3:0] a, b, output [4:0] s);
assign s = a + b;
endmodule
```

- Add and adapt the constraints file Nexysx.UCF
- Generate the configuration file and test the circuit.